
Signals and Systems

Matlab Homework #3

Table of Contents

Introduction	1
Initialize Variables	1
Part 1: Complex Exponential Input	1
Part 2 Bode Plot	5
Part 3: DC to AC Converter	7
Part 3C: Power Efficiency	8
Part 3B : Bode Plot	9

Introduction

- Author: Will Burgess
- Class: ESE 351
- Date: Created 2/11/2024, Last Edited 2/20/2024
- With contributions from: Mack Larosa, Tasha Igic, Mischa Tranor

Initialize Variables

```
close all
R = 1e3; %Resistance in ohms
C = 5e-6; %Capacitance in Farads
tau = R*C;
sampleFreq = 44.1e3;
samplePeriod = 1/sampleFreq;
```

Part 1: Complex Exponential Input

```
freqVals = [10, 1000];

for i = 1:2
    freq = freqVals(i);
    angularFreq = 2*pi*freq;

    sampleTimes = 0:samplePeriod:15*(1/freq);
    %inputFunct = zeros(1,length(timePoints));
    inputFunct = exp(1j*angularFreq*sampleTimes);
```

```
%LCCDE Lowpass

lsim_Lo = lsim(1/tau , [1 ,1/tau], inputFuncnt,sampleTimes);

%LCCDE Highpass

lsim_Hi = lsim([1 0] , [1 ,1/tau], inputFuncnt,sampleTimes);

% Create subplots
%plot lowpass
figure;
hold on
subplot(3, 1, 1);
plot(sampleTimes, abs(inputFuncnt), 'b', sampleTimes, abs(lsim_Lo), 'r');
title('Magnitude');
xlabel('Time(s)');
ylabel('Output');
legend('Input', 'Output');

subplot(3, 1, 2);
plot(sampleTimes, real(inputFuncnt), 'b', sampleTimes, real(lsim_Lo), 'r');
title('Real Part');
xlabel('Time(s)');
ylabel('Output');
legend('Input', 'Output');

subplot(3, 1, 3);
plot(sampleTimes, imag(inputFuncnt), 'b', sampleTimes, imag(lsim_Lo), 'r');
title('Imaginary Part');
legend('Input', 'Output');
xlabel('Time(s)');
ylabel('Output');
sgtitle(['Lowpass Exponential Responses: Frequency = ',
num2str(freq), 'Hz']);


hold off
% plot highpass
figure;
hold on
subplot(3, 1, 1);
plot(sampleTimes, abs(inputFuncnt), 'b', sampleTimes, abs(lsim_Hi), 'r');
title('Magnitude');
xlabel('Time(s)');
ylabel('Output');
legend('Input', 'Output');

subplot(3, 1, 2);
plot(sampleTimes, real(inputFuncnt), 'b', sampleTimes, real(lsim_Hi), 'r');
title('Real Part');
xlabel('Time(s)');
ylabel('Output');
legend('Input', 'Output');


subplot(3, 1, 3);
```

```
plot(sampleTimes, imag(inputFunc), 'b', sampleTimes, imag(lsim_Hi), 'r');  
title('Imaginary Part');  
xlabel('Time(s)');  
ylabel('Output');  
legend('Input', 'Output');  
sgtitle(['Highpass Exponential Responses: Frequency = ',  
num2str(freq), 'Hz']);  
end
```

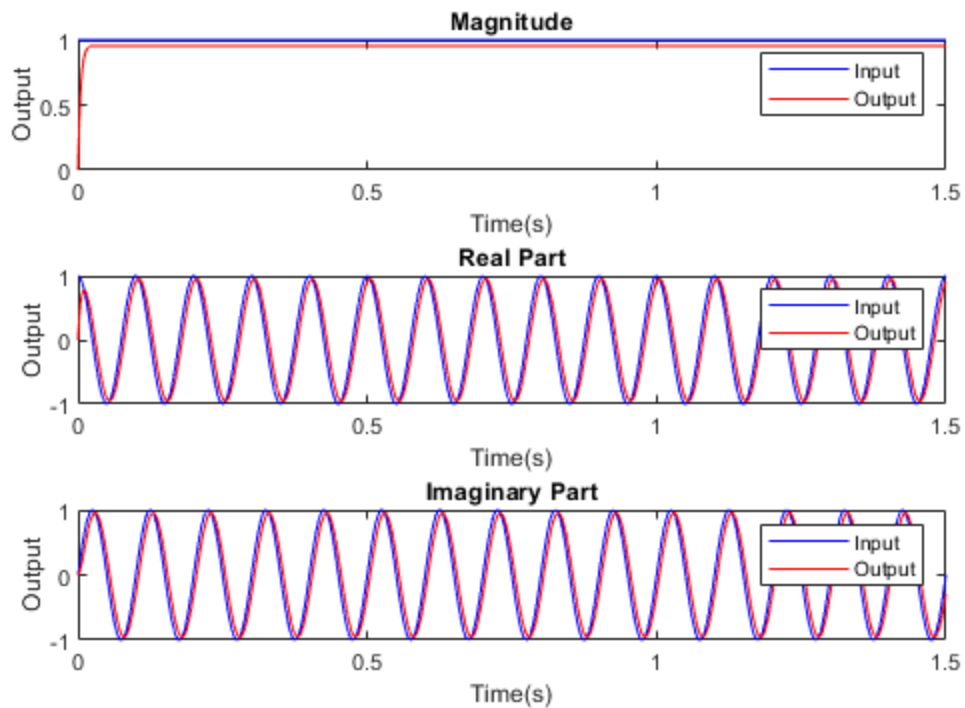
Lowpass Exponential Responses: Frequency = 10Hz



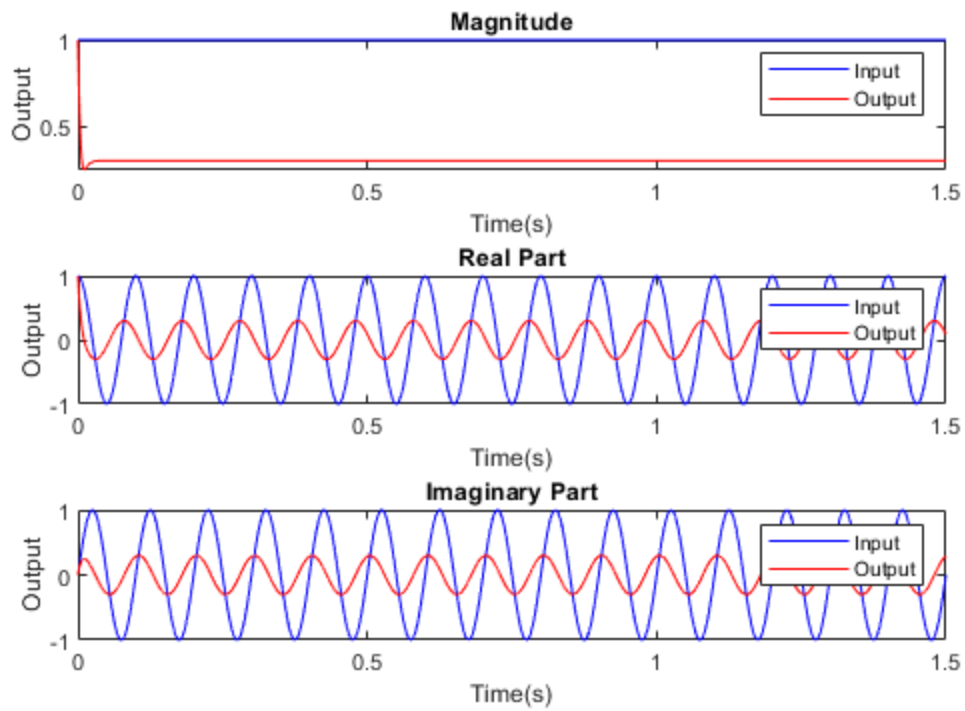
Highpass Exponential Responses: Frequency = 10Hz



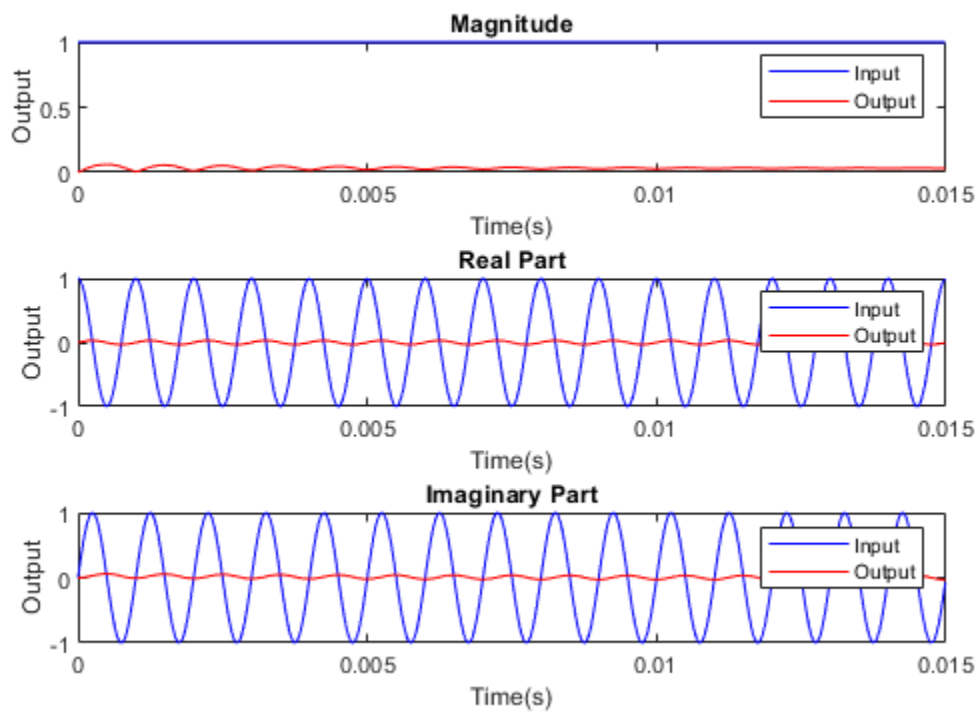Lowpass Exponential Responses: Frequency = 1000Hz



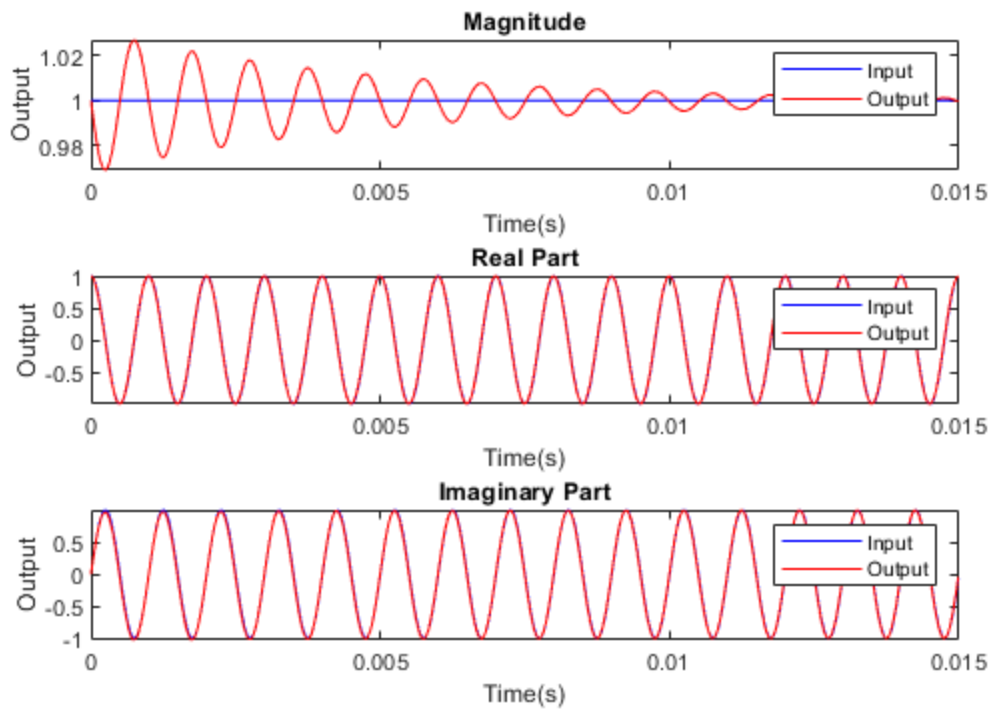Highpass Exponential Responses: Frequency = 1000Hz



Part 2 Bode Plot

```
freqRange = logspace(1,4,100);
sampleTimes = 0:samplePeriod:2; %Sim to 2s for better steady state

H_Hi = zeros(length(freqRange),1);
H_Lo = zeros(length(freqRange),1);

for i = 1:length(freqRange)
    angularFreq = freqRange(i);
    inputFunct = exp(1j*angularFreq*sampleTimes);

    %Lsim Lowpass
    lsim_Lo = lsim(1/tau , [1 ,1/tau], inputFunct,sampleTimes);

    %Lsim Highpass
    lsim_Hi = lsim([1 0] , [1 ,1/tau], inputFunct,sampleTimes);

    % Compute H, assume steady state at index 660
    H_Lo(i) = lsim_Lo(end) / inputFunct(end);
    H_Hi(i) = lsim_Hi(end) / inputFunct(end);
    % Compute magnitude in dB and phase normalized by pi
end
```

```
%Calc for Highpass
mag_Hi = 20*log10(abs(H_Hi));
phase_Hi = angle((H_Hi)/pi);

%Calc for Lowpass
mag_Lo = 20*log10(abs(H_Lo));
phase_Lo = angle((H_Lo)/pi);


%Plot
figure;
hold on
subplot(4, 1, 1);
semilogx(freqRange, mag_Lo, LineWidth=1.5);
title('Lowpass Magnitude');
xlabel('Frequency (Hz)');
ylabel('Output (dB)');

subplot(4, 1, 2);
semilogx(freqRange, mag_Hi, LineWidth=1.5);
title('HighPass Magnitude');
xlabel('Frequency (Hz)');
ylabel('Output (dB)');

subplot(4, 1, 3);
semilogx(freqRange, phase_Lo, LineWidth=1.5);
title('LowPass Phase');
xlabel('Frequency (Hz)');
ylabel('Output Phase (Radians)');

subplot(4, 1, 4);
semilogx(freqRange, phase_Hi, LineWidth=1.5);
title('HighPass Phase');
xlabel('Frequency (Hz)');
ylabel('Output Phase (Radians)');
sgtitle('Bode Plot Outputs of High and Lowpass Filters with Varying
Frequency');
hold off
```

Bode Plot Outputs of High and Lowpass Filters with Varying Frequency

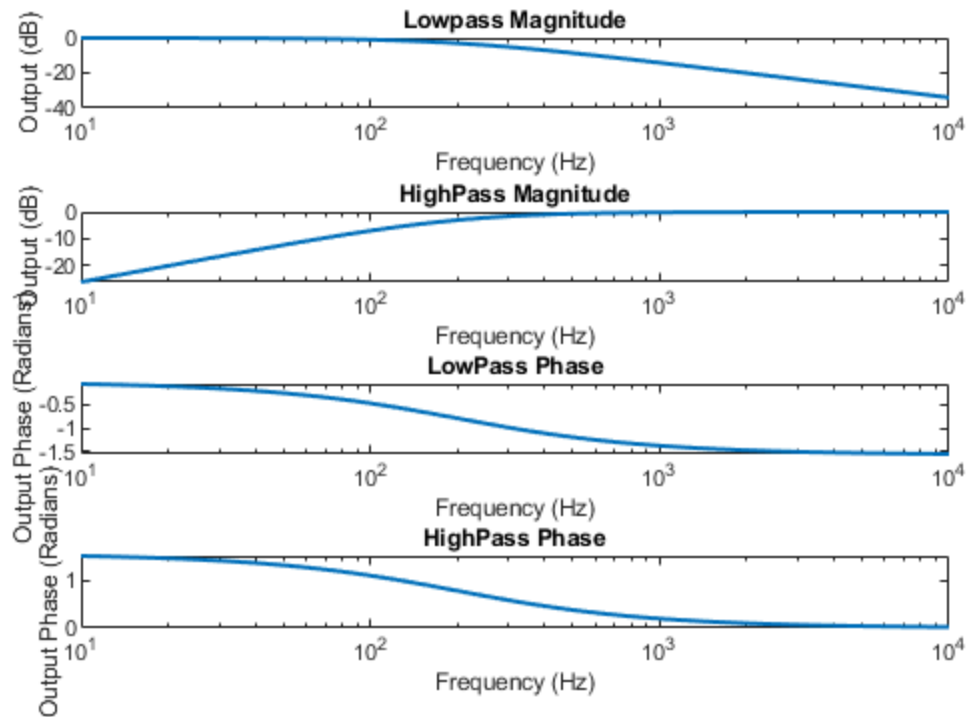

Part 3: DC to AC Converter


Define parameters

```
sampleFreq = 10e3;  
samplePeriod = 1/sampleFreq;  
frequency = 60;      % Desired frequency in Hz  
  
cutoff = 160;  
C = 10e-6;  
R = 1/(2*pi*cutoff*C);  
tau = R*C;  
  
sampleTimes = 0:samplePeriod:20*(1/frequency);  
  
% Generate square wave  
sq = square(2*pi*frequency*sampleTimes);  
inputFunct = sq;  
  
%Filter Coeffs  
a = [1, samplePeriod/tau-1];  
b = samplePeriod/tau;  
  
% Pass signal through RC Lowpass filter 6 separate times  
output = zeros(size(inputFunct));  
for i = 1:6
```

```
output = filter(b, a, inputFuncnt);

inputFuncnt = output;
end

% Plot the output
figure()
hold on
plot(sampleTimes, sq);
plot(sampleTimes, output);
xlabel('Time (s)')
ylabel('Output (V)')
title('DC to AC Converter')
legend('Input', 'Output');
hold off
```

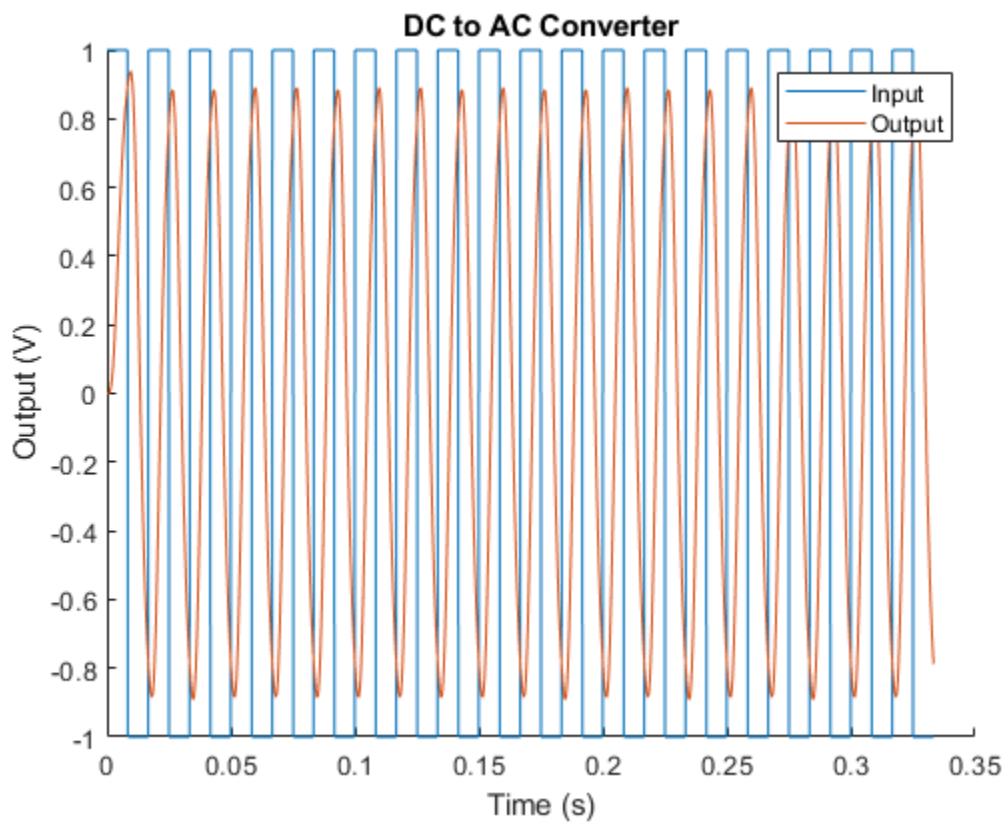

Part 3C: Power Efficiency

```
%Cut off first initial spike of the power, only interested in steady state
sq = sq(1000:end);
output = output(1000:end);
Pin = sum(sq(1:end).^2);
Pout = sum(output(1:end).^2);

efficiency = Pout/Pin;
fprintf('Efficiency Via Integral: %f\n', efficiency*100)
```



```
% al for the sinc function is
% power efficiency = (2a1)^2/Pin
% Pin = 1
a = 7/6*pi;
fprintf('Theoretical Max Efficiency Via Fourier Series: %f\n', (2*a)^2)
```

Efficiency Via Integral: 39.781441

Theoretical Max Efficiency Via Fourier Series: 53.734513

Part 3B : Bode Plot

```
sampleTimes = 0:samplePeriod:0.5; %2 seconds

frequencyRange = logspace(1,4,100);

H = zeros(size(frequencyRange));
for i = 1:length(frequencyRange)

    squareInput = exp(1i*frequencyRange(i)*sampleTimes);

    outputForBode = squareInput;
    for n = 1:6 % 6 low pass filters
        outputForBode = lsim(1/tau,[1 1/tau],outputForBode,sampleTimes);
    end


    H(i) = outputForBode(end)/squareInput(end);

end
mag = 20*log(abs(H));


ang = angle(H/pi);

figure;
hold on
subplot(2, 1, 1);
semilogx(freqRange, mag, LineWidth=1.5);
title('Bode Magnitude');
xlabel('Frequency (Hz)');
ylabel('Output (dB)');

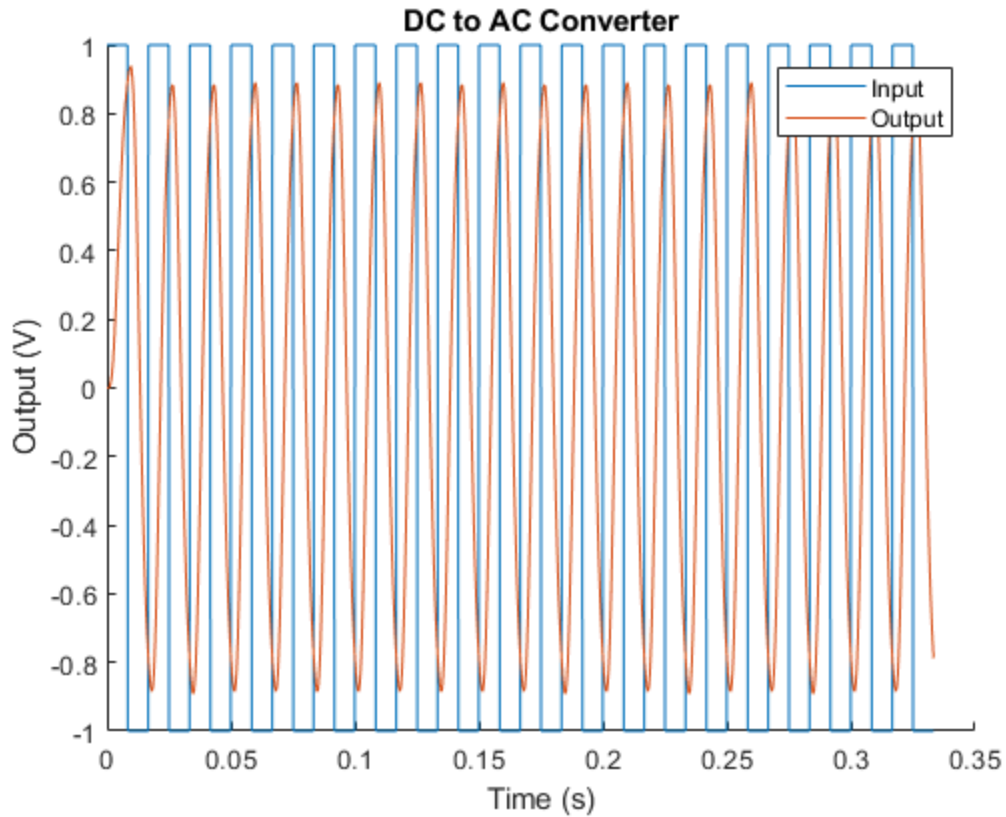subplot(2, 1, 2);
semilogx(freqRange, ang, LineWidth=1.5);
title('Bode Phase');
xlabel('Frequency (Hz)');
ylabel('Output (Radians)');
sgtitle('Bode Plot Output of DC to AC Converter with Varying Frequency');
hold off
```



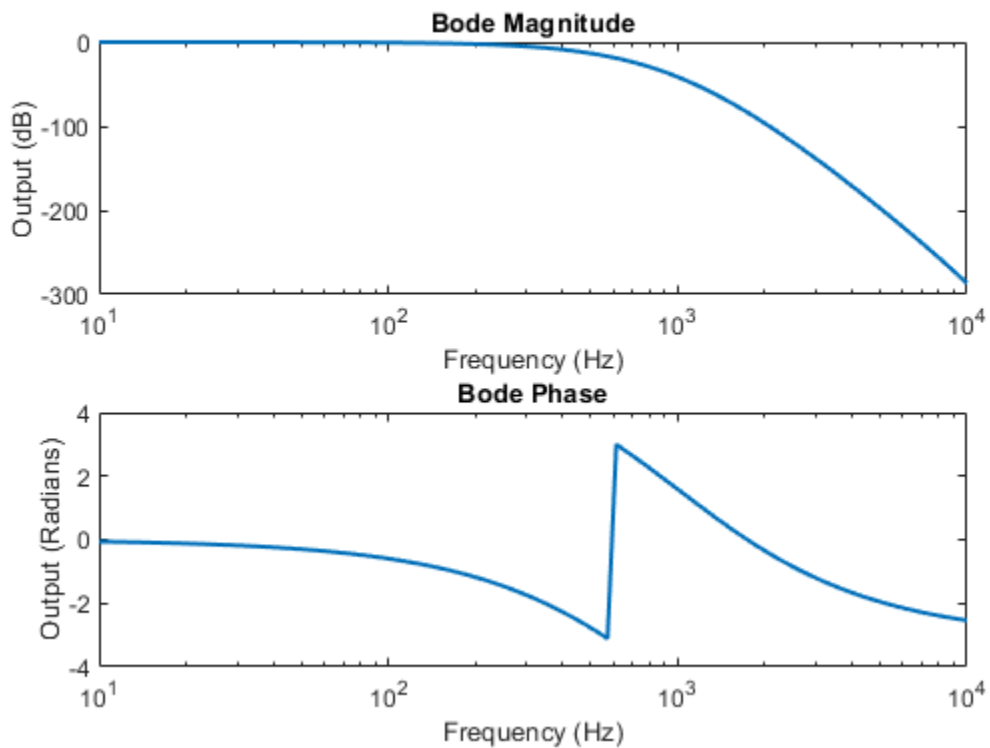Bode Plot Output of DC to AC Converter with Varying Frequency



Published with MATLAB® R2022a